

II B.Tech I Semester Regular Examinations, November 2008
SWITCHING THEORY AND LOGIC DESIGN
 (Common to Electrical & Electronic Engineering, Electronics &
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &
 Control Engineering, Electronics & Computer Engineering and
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) What is the Gray code? What are the rules to construct Gray code? Develop the 4 bit Gray code for the decimal 0 to 15.
 (b) List the XS3 code for decimal 0 to 9.
 (c) What are the rules for XS3 addition? Add the two decimal numbers 123 and 658 in XS3 code. [8+2+6]

2. (a) State Duality theorem. List Boolean laws and their Duals.
 (b) Simplify the following Boolean functions to minimum number of literals:
 i. $F = ABC + ABC' + A'B$
 ii. $F = (A+B)' (A'+B')$.
 (c) Realize XOR gate using minimum number of NAND gates. [8+4+4]

3. Simplify the following Boolean expressions using K-map and implement them using NOR gates:
 (a) $F(A, B, C, D) = AB'C' + AC + A'CD'$
 (b) $F(W, X, Y, Z) = W'X'Y'Z' + WXY'Z' + W'X'YZ + WXYZ$. [16]

4. (a) Design BCD to Gray code converter and realize using logic gates.
 (b) Design 2*4 decoder using NAND gates. [10+6]

5. (a) Draw the basic macro cell logic diagram and explain.
 (b) Explain the general CPLD configuration with suitable block diagram. [16]

6. (a) Draw the logic diagram of a 4 bit binary ripple counter using positive edge triggering.
 (b) Draw the block diagram of a 4 - bit serial adder and explain its operation. [16]

7. (a) Write the differences between Mealy and Moore type machines.
 (b) A sequential circuit has 2 inputs $w_1=w_2$ and an output z . It's function is to compare the i/p sequence on the two i/p's. If $w_1=w_2$ during any four consecutive clock cycles, the circuit produces $z=1$ otherwise $z=0$
 $w_1 = 0110111000110$
 $w_2 = 1110101000111$
 $z = 0000100001110$ [8+8]

8. (a) For the given control state diagram obtain its equivalent ASM chart.
(b) Design control logic circuit as shown in figure 8b using multiplexers. [8+8]

 


Figure 8b

II B.Tech I Semester Regular Examinations, November 2008
SWITCHING THEORY AND LOGIC DESIGN
 (Common to Electrical & Electronic Engineering, Electronics &
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &
 Control Engineering, Electronics & Computer Engineering and
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Why the binary number system is used in computer design?
 (b) Given the binary numbers
 $a = 1010.1$, $b = 101.01$, $c = 1001.1$ perform the following:
 - i. $a + c$
 - ii. $a - b$
 - iii. $a . c$
 - iv. a / b .
 (c) Convert $(2AC5.D)_{16}$ to binary and then to octal. [2+10+4]
2. (a) Simplify the following Boolean functions to minimum number of literals:
 - i. $(a + b)' (a' + b)'$
 - ii. $y(wz' + wz) + xy$
 (b) Prove that AND-OR network is equivalent to NAND-NAND network.
 (c) State Duality theorem. List Boolean laws and their Duals. [4+4+8]
3. (a) What are don't-care conditions? Explain its advantage with example.
 (b) Simplify the following Boolean function for minimal POS form using K-map and implement using NOR gates.
 $F(W,X,Y,Z) = \pi(4,5,6,7,8,12) . d(1,2,3,9,11,14)$ [4+12]
4. (a) Design BCD to Gray code converter and realize using logic gates.
 (b) Design 2^*4 decoder using NAND gates. [10+6]
5. (a) Using PLA logic, implement a BCD to excess 3 code converter. Draw its truth table and logic diagram.
 (b) Discuss about types of sequential PCDs. [16]
6. (a) What do you mean by triggering. Explain the various triggering modes with examples.
 (b) Draw the logic diagram of a JK flip flop and using excitation table, explain its operation. [16]

7. (a) Derive a circuit that realises the FSM defined by the state assigned table in figure below using JK flip flops.

Present State	Next state		Output
	w=0	w=1	
y_2y_1	y_2y_1	$y_2 y_1$	Z
00	10	11	0
01	01	00	0
10	11	00	0
11	10	01	1

- (b) Find the state table for the following state diagram as shown in figure 7b of a simple sequential ckt. [8+8]

 


Figure 7b

8. (a) For the given control state diagram, draw the equivalent ASM chart as shown in figure 8a.

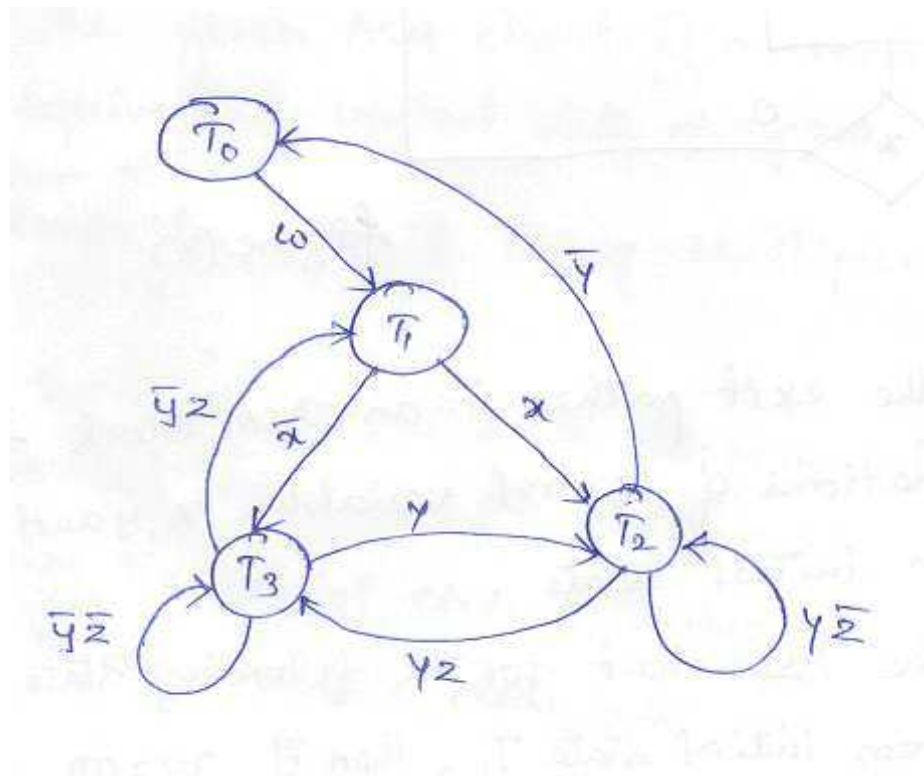


Figure 8a

Code No: 07A3EC03

Set No. 2

(b) Design the control circuit using multiplexers for the above state diagram. [8+8]

II B.Tech I Semester Regular Examinations, November 2008
SWITCHING THEORY AND LOGIC DESIGN
 (Common to Electrical & Electronic Engineering, Electronics &
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &
 Control Engineering, Electronics & Computer Engineering and
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) What is the necessity of binary codes in computers?
 (b) Encode the decimal numbers 0 to 9 by means of the following weighted binary codes.
 - i. 8 4 2 1
 - ii. 2 4 2 1
 - iii. 6 4 2 -3
 (c) Determine which of the above codes are self complementing and why? [2+12+2]
2. (a) List the Minterms and Maxterms for three binary variables. Draw the truth table and express the Boolean function $F(A,B,C)$ whose minterms are 1,3,5,7 as Canonical Sum of Minterms form.
 (b) Simplify the following Boolean functions to minimum number of literals:
 - i. $F = X'Y' + XYZ + X'Y$
 - ii. $F = X + Y[Z + (X+Z)']$
 (c) For the logic expression $Y = AB' + A'B$:
 - i. Obtain the truth table.
 - ii. Name the operation performed.
 - iii. Realize this using AND, OR, NOT gates. [8+4+4]
3. Simplify the following Boolean expressions using K-map and implement them using NOR gates:
 - (a) $F(A, B, C, D) = AB'C' + AC + A'CD'$
 - (b) $F(W, X, Y, Z) = W'X'Y'Z' + WXY'Z' + W'X'YZ + WXYZ$. [16]
4. (a) Implement Full Adder using decoder and OR gates.
 (b) Realize the Boolean function $T(X,Y,Z) = \Sigma(1,3,4,5)$ using logic gates for **hazard free**. [8+8]
5. (a) List the PLA programming table for the BCD to excess-3 code converter.
 (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-volt power supply. How many pins are needed for the integrated circuit package? Draw the block diagram of this ROM. [8+8]

6. (a) Draw the ckt diagram of 4 bit ring ring counter using D flipflops and explain its operation with the help of bit pattern.
 - (b) Distinguish b/w transition table and excitation table? [16]

7. Explain the following related to sequential ckts with suitable examples.
 - (a) State diagram
 - (b) State table
 - (c) State assignment. [16]

8. (a) For the given control state diagram obtain its equivalent ASM chart.
 - (b) Design control logic circuit as shown in figure 8b using multiplexers. [8+8]

 


Figure 8b

II B.Tech I Semester Regular Examinations, November 2008
SWITCHING THEORY AND LOGIC DESIGN
(Common to Electrical & Electronic Engineering, Electronics &
Instrumentation Engineering, Bio-Medical Engineering, Electronics &
Control Engineering, Electronics & Computer Engineering and
Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain the 7 bit Hamming code.
(b) A receiver with even parity Hamming code is received the data as 1110110.
Determine the correct code. [10+6]
2. (a) State and prove the following Boolean laws:
 - i. Commutative
 - ii. Associative
 - iii. Distributive.(b) Find the complement of the following Boolean functions and reduce them to minimum number of literals:
 - i. $(bc' + a'd)(ab' + cd')$
 - ii. $b'd + a'bc' + acd + a'bc$(c) Which gate can be used as parity checker? Why? [6+8+2]
3. (a) List the Boolean function simplification rules in the K-map
(b) Simplify the following Boolean function for minimal SOP form using K-map and implement using NAND gates.
 $F(W,X,Y,Z) = \Sigma(1,3,7,11,15) + d(0,2,5)$ [4+12]
4. Design a combinational circuit that converts a decimal digit from 2,4,2,1 code to 8, 4,-2,-1 code. [16]
5. (a) The following memory units are specified by the no of words times the number of bits per word. How many address lines and input-output data lines are needed in each case?
 - i. $4K \times 16$
 - ii. $2G \times 8$
 - iii. $16M \times 32$
 - iv. $256K \times 64$.(b) Give the number of bytes stored in the memories listed above. [16]
6. (a) Distinguish between a state table and a flow table?

- (b) Draw the logic diagram and write functional table of an SR latch using NAND gates. Explain the operation. [16]

7. For the given minimal state - table:

- (a) Give proper assignment.
 (b) And design the circuit using D - Flip-flops. [6+10]

Present State	Next state,		out - put	
	X=0	X=1	X=0	X =1 (Z)
q_1	q_2	q_1	0	0
q_2	q_3	q_1	0	0
q_3	q_4	q_5	0	0
q_4	q_4	q_1	0	0
q_5	q_2	q_1	1	0

8. (a) How do you indicate moore outputs and mealy outputs in an ASM block.
 (b) Obtain the ASM chart for the following state transition.
 Start for State T_1 ; then if $xy=00$, go to T_2 if $xy=01$, go to T_3 ; if $xy=10$ go to T_1 ; otherwise go to T_3 . [8+8]
