

I B.Tech Regular Examinations, May/Jun 2008

## NETWORK ANALYSIS

( Common to Electronics & Communication Engineering, Electronics & Instrumentation Engineering, Bio-Medical Engineering, Electronics & Control Engineering, Electronics & Telematics and Electronics & Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. A circuit consisting of three resistances  $12\ \Omega$ ,  $18\ \Omega$  and  $36\ \Omega$  respectively joined in parallel is connected in series with a fourth resistance. The whole circuit is applied with  $60\text{V}$  and it is found that the power dissipated in the  $12\ \Omega$  resistor is  $36\ \text{W}$ . Determine the value of the fourth resistance and the total power dissipated in the circuit. [16]
2. Derive expression for R.M.S. and average value of a sinusoidal alternating quantity. [16]
3. An impedance  $Z_1 = 10 + j10\ \Omega$  is connected in parallel with another impedance of resistance  $8.5\ \Omega$  and a variable capacitance connected in series. Find  $C$  such that the circuit is in resonance at  $5\ \text{KHz}$ . [16]
4. For the network shown in figure 4 draw oriented graph and draw all possible trees. [16]

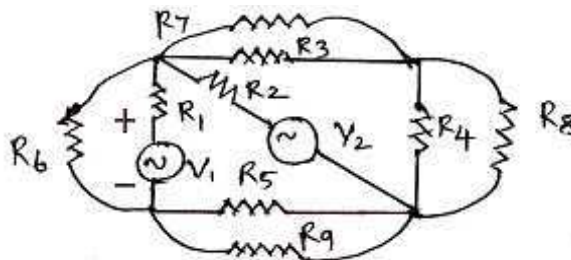


Figure 4

5. Using Norton's theorem, find the current through the load impedance  $Z_L$ , for the network as shown in figure 5. [16]

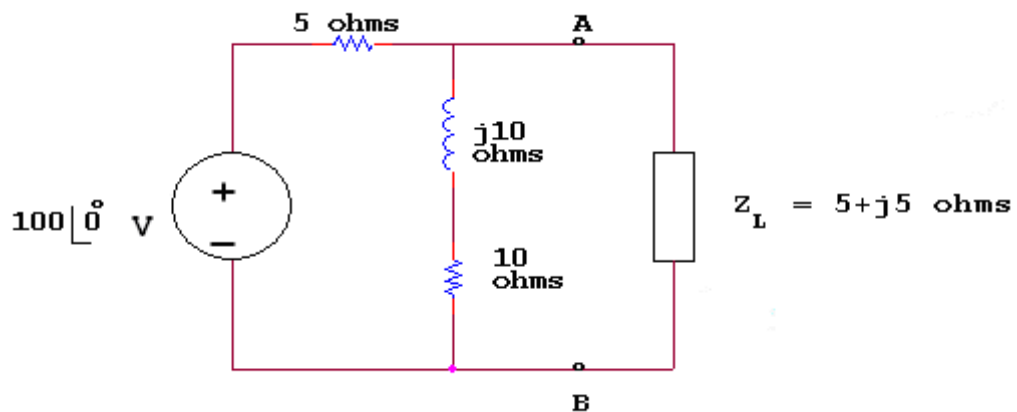


Figure 5

6. For the two port network shown in the figure 6, the currents  $I_1$  and  $I_2$  entering at port 1 and 2 respectively are given by the equations.

$$I_1 = 0.5 V_1 - 0.2 V_2$$

$$I_2 = -0.2V_1 + V_2$$

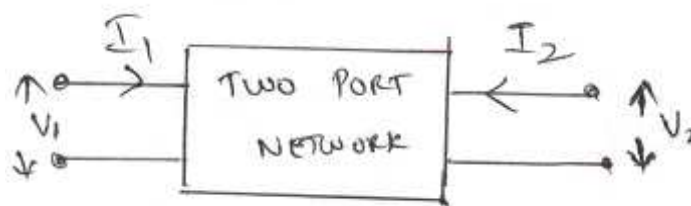


Figure 6

Where  $V_1$  and  $V_2$  are the port voltages at port 1 and 2 respectively. Find the Y, Z, ABCD parameters for the network. Also find its equivalent  $\Pi$  network. [16]

7. Derive the transient response of RLC series circuit with unit step input. [16]
8. Design a symmetrical T attenuator to give 20 db attenuation to have a characteristic impedance of  $75 \Omega$ . [16]

\*\*\*\*\*

I B.Tech Regular Examinations, May/June 2008

## NETWORK ANALYSIS

( Common to Electronics & Communication Engineering, Electronics & Instrumentation Engineering, Bio-Medical Engineering, Electronics & Control Engineering, Electronics & Telematics and Electronics & Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. A circuit consists of three resistors 3 ohms, 4 ohms and 6 ohms in parallel and a fourth resistor 4 ohms in series. A battery of emf 12 V and internal resistance 6 ohms is connected across the circuit. Find the total current in the circuit and terminal voltage across the battery. [16]
2. A metal filament lamp, rated at 750 Watts, 100V is to be connected in series with a capacitor across a 230V, 60 Hz supply. Calculate [16]
  - (a) The capacitance required
  - (b) The power factor.
3. Determine the value of the capacitance C in order that the circuit in the figure 3 is resonant at 6366 Hz. [16]

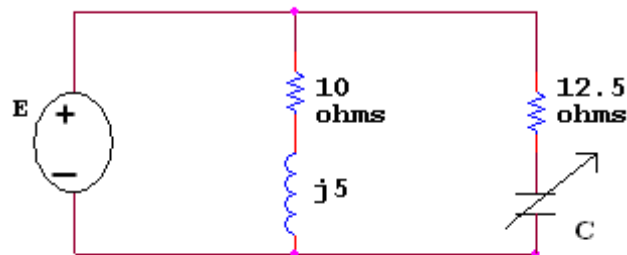


Figure 3

4. For the network shown in figure 4 find the tie-set matrix loop current. [16]

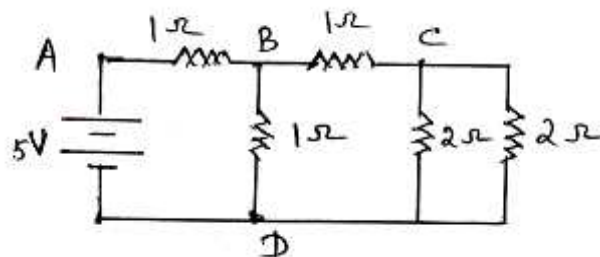


Figure 4

5. Use Thevenin's Theorem and find the current through  $(5+j4)$  ohms impedance, for the network as shown in figure 5. [16]

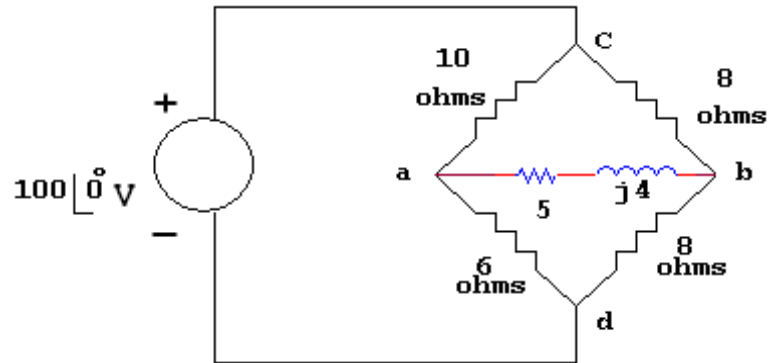


Figure 5

6. Determine the Z parameters of the network shown in figure 6. [16]

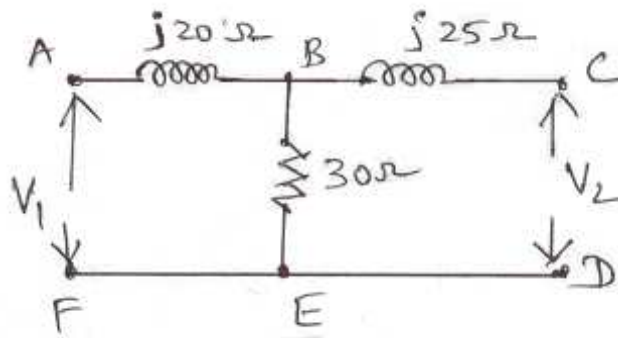


Figure 6

7. Derive the transient response of RLC series circuit with unit step input. [16]
8. Design a composite high pass filter to operate into a load of 600 ohms and have a cutoff frequency of 1.2 kHz. The filter is to have one constant K section, one m-derived section with infinite frequency of 1.1kHz and suitable termination half section. [16]

\*\*\*\*\*

I B.Tech Regular Examinations, May/June 2008

## NETWORK ANALYSIS

( Common to Electronics & Communication Engineering, Electronics & Instrumentation Engineering, Bio-Medical Engineering, Electronics & Control Engineering, Electronics & Telematics and Electronics & Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- Derive the expression for energy stored in an inductor.
  - A 50 ohm resistor is in parallel with a 100 ohm resistor. The current in 50 ohm resistor is 7.2A. What is the value of third resistance to be added in parallel to make the line current as 12.1A? [6+10]
- Define
    - frequency,
    - phase
    - form factor and
    - peak factor
  - Explain the term phase difference. [4×3+4]
- Write down the relationship between phase voltage and line voltage and phase current and line current in a delta connected circuit.
  - Draw a 3 phase sinusoidal voltage system waveform with RYB sequence.
  - Draw the phasor diagram for delta and star connected loads. [6+5+5]
- Write the matrix loop equation for the network shown in figure 4 and determine the loop currents. [16]

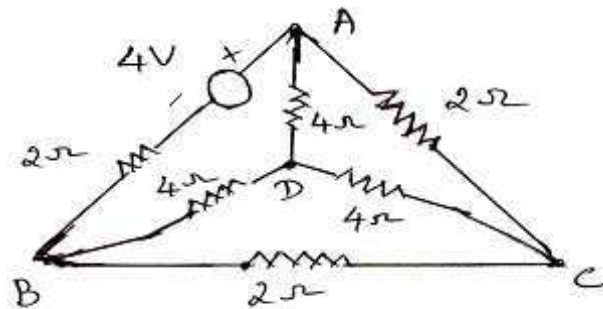


Figure 4

- Find  $V_a$  using Super position principle in the circuit shown in the figure 5. [16]

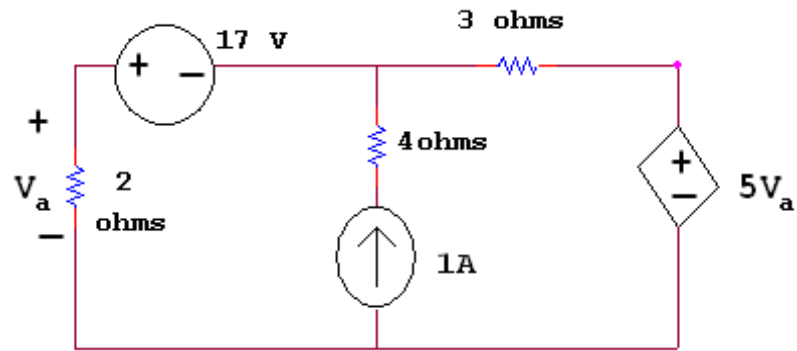


Figure 5

6. Find the Y - parameters of the network shown in figure 6: [16]

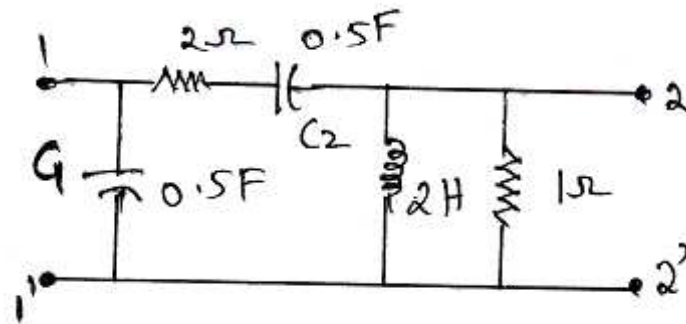


Figure 6

7. In the circuit shown in figure 7,  $E_g(t) = 2.5 t$  Volts. What are the values of  $i(t)$  and  $V_L(t)$  at  $t = 4$  seconds. [16]

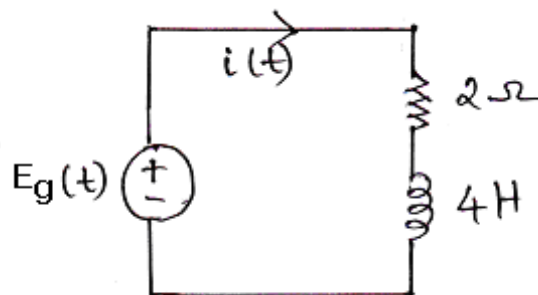


Figure 7

8. Design a symmetrical T-attenuation to give 20 dB attenuation and to have characteristic impedance of  $300\Omega$ . [16]

\*\*\*\*\*

**I B.Tech Regular Examinations, May/Jun 2008**  
**NETWORK ANALYSIS**

( Common to Electronics & Communication Engineering, Electronics & Instrumentation Engineering, Bio-Medical Engineering, Electronics & Control Engineering, Electronics & Telematics and Electronics & Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) State Ohm's law and Kirchoff's voltage law.
- (b) Obtain the potential difference  $V_{AB}$  in the circuit shown in figure 1 using Kirchoff's laws. [6+10]

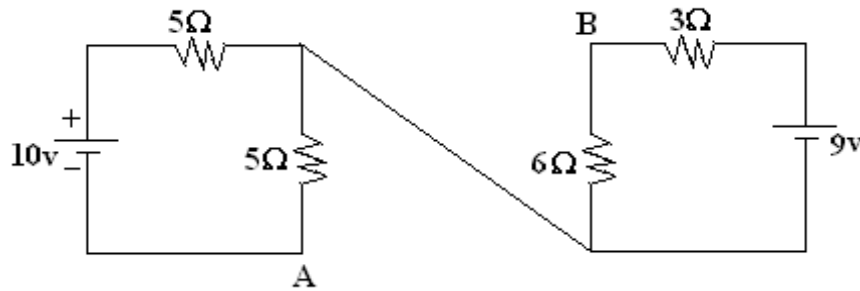


Figure 1

2. A current  $i = 4 \sin (314t - 100)$  produces a voltage drop  $v = 220 \sin (314t - 200)$  in a circuit. Find the values of the circuit parameters assuming a series circuit. [16]
3. Three impedances, each consisting of  $20\Omega$  resistance and  $15 \Omega$  inductive reactance in series, connected in star, are across a 400V, 3 phase supply. Calculate
  - (a) line current
  - (b) phase current
  - (c) total power consumed
  - (d) power factor of the load. Also draw the phasor diagram. [16]
4. For the graph in the figure 4, write the cut set schedule and obtain the relation between tree branch voltages and branch voltages. [16]

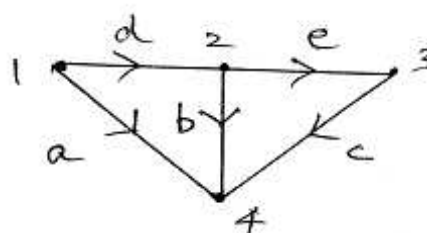


Figure 4

5. (a) State and explain Thevenin's Theorem.  
 (b) What are the limitations of Thevenin's Theorem.  
 (c) Explain the steps to apply Thevenin's Theorem and draw the Thevenin's equivalent circuit. [6+4+6]

6. For the two port network shown in the figure 6, the currents  $I_1$  and  $I_2$  entering at port 1 and 2 respectively are given by the equations.

$$I_1 = 0.5 V_1 - 0.2 V_2$$

$$I_2 = -0.2V_1 + V_2$$

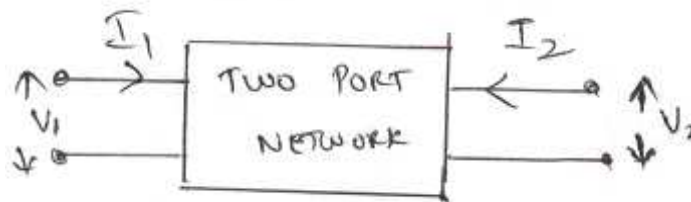


Figure 6

Where  $V_1$  and  $V_2$  are the port voltages at port 1 and 2 respectively. Find the Y, Z, ABCD parameters for the network. Also find its equivalent  $\Pi$  network. [16]

7. In a series RL circuit, with  $R = 3\Omega$  &  $L = 1H$ , a D.C. Voltage of  $E = 50V$  is applied at  $t=0$ . Find the transient response of current. Plot the response also. [16]
8. Design a m-derived HPF with a cut-off frequency of 10KHz. Design impedance of  $500\Omega$  and  $m = 0.4$ . [16]

\*\*\*\*\*