

Code No: E315

OR

II B.Tech.(CCC) Supplementary Examinations, June 2008
INDUSTRIAL ELECTRONICS
(Mechanical Engineering)

Time: 3 hours

Max Marks: 100

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Explain the phenomenon of "Hall Effect"
What are the applications of Hall Effect.
- (b) Draw the circuit of Half wave rectifier with resistance load and explain the working of it giving input and output wave forms. [10+10]
2. (a) List different types of voltage Regulators. Draw the circuit of series voltage Regulator and explain the working of it.
- (b) What are the different methods of Triggering S C R. Explain one of these methods. [10+10]
3. (a) Describe the Gate control method in Controlled rectifiers with SCR.
- (b) Draw FET R-C coupled amplifier and explain the working of it.
- (c) Write a brief note on "Frequency stability in oscillators. [8+8+4]
4. (a) Describe the construction and working of a photo-diode
- (b) Draw and discuss its Volt - ampere characteristics
- (c) List different methods of digital system displays. [10+5+5]
5. (a) Compare and contrast the following timers
 - i. Thermal Timers
 - ii. Electromechanical Timers
 - iii. Mechanical Timers
 - iv. Electrochemical Timers
- (b) Explain
 - i. Bimetal strip Timers
 - ii. Thermal expansion Timers. [10+10]
6. (a) Explain the principle of Dielectric heating
- (b) Explain the application of Induction heating for Brazing
- (c) Explain one method of generation of ultrasonic waves. [6+6+8]
7. (a) Explain what is meant by a thermocouple.
- (b) Give a typical method, in detail, for the measurement of temperature using a thermocouple. [5+15]

Code No: E315

OR

8. Draw a block diagram of an electronic analog computer and explain each block for the differential equation $\frac{d^2v}{dt^2} + k_1 \frac{dv}{dt} + k_2 v - v_1 = 0$. [20]
