

Code No. B4303

NR

JAWAHARLAL NEHRU TECHNOLOGY UNIVERSITY, HYDERABAD

M .Tech. II Semester Supplementary Examinations, March – 2009

FLEXIBLE AC TRANSMISSION SYSTEMS

**(Common to Power Electronics & Electric Drives, Power Electronics,
Electrical Power Engineering, Power Engineering & Energy Systems and
Power Systems (High Voltage))**

Time: 3 hours

Max. Marks.60

**Answer any Five questions
All questions carry equal marks**

- 1.a) What are the loading capability limitations? Explain how they can limit the loading capability?
- b) Explain relative importance of controllable parameters.
- 2.a) Explain transformer connections for 12-pulse operation.
- b) Explain operation of three-phase full wave bridge converter?
- 3.a) Explain operation of PWM converter with wave forms.
- b) Explain basic concept of current sourced converter.
- 4.a) What are the objectives of shunt compensation? Explain how shunt compensation is used for voltage regulation at the midpoint to segment the transmission line?
- b) Explain, how shunt compensation will increase the transient stability?
- 5.a) Explain the operation of Thyristor-controlled reactor?
- b) Explain the Hybrid VAR generation with their operating V-I areas.
- 6.a) What is the regulation slope? What are the reasons for regulation slope? Explain with V-I characteristics of the SVC and STATCOM?
- b) Derive transfer function and explain dynamic performance of Static VAR compensation.
- 7.a) Explain the concept of series capacitive compensation?
- b) Explain, how series compensation is used for improvement of transient stability?
- 8.a) Explain control schemes for GSC and TCSC.
- b) Explain the operation of GTO Thyristor-controlled series capacitor.
