

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
II.B.TECH - I SEMESTER REGULAR EXAMINATIONS NOVEMBER, 2009
DIGITAL LOGIC DESIGN
(Common to CSE, IT, CSS)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
 All questions carry equal marks

- - -

1. a) Convert the following to require form
 - i) $(163.789)_{10} = (\quad)_8$
 - ii) $(101101110001.00101)_2 = (\quad)_8$
 - iii) $(292)_{16} = (\quad)_2$
 b) Find the difference of $(3250 - 72546)_{10}$ by using 10's complement.
 c) What is meant by self complementing codes. [16]

2. a) Obtain the minimal sum of product expression of given function by using consensus theorem.

$$f = \overline{ABC} + \overline{ABC} + BCD + \overline{ACD}$$
 b) Which of the following statements are true? Justify.
 - i) If $A+B+C = C+D$ then $A+B = D$
 - ii) If $A+B = C$ then $\overline{AD} + \overline{BD} = \overline{CD}$ [8+8]

3. a) Design a circuit which finds the 2'S complement of a 4 bit binary number. Write HDL program for this design.
 b) Prove that NAND and NOR operations are commutative but not Associative. [8+8]

4. a) Design a BCD to Gray code converter using 8:1 MUXS.
 b) Write a HDL program to model an 8 bit comparator using 2 bit comparators. [8+8]

5. a) Draw a neat circuit diagram of positive triggered D flip flop and explain its operation.
 b) Design a master slave JK flip flop by writing HDL program to describe the flip flop. [8+8]

6. a) Design a 4 bit Ripple counter using T flip flop. Explain using wave forms.
 b) Write HDL program in behaviour model to design a 4 bit shift left register. [8+8]

7. a) Design a Hamming code encode to obtain 11 bit code from the circuit use PLAS.
 b) Write a brief note on ROMS. [8+8]

8. a) Design an asynchronous sequential circuit with the following excitation requirement and output functions

$$Y_1 = x_1x_2 + x_1\overline{y_2} + \overline{x_2}y_1$$

$$Y_2 = x_2 + x_1\overline{y_1}y_2 + \overline{x_1}y_1$$

$$Z = x_2 + y_1$$

- b) Design a hazard free circuit to implement $y = (x_1 + x_2)(x_2 + x_3)$ [8+8]
