

Code No: 52204/MT

M.Tech. – II Semester Regular Examinations, September, 2008

FLEXIBLE AC TRANSMISSION SYSTEMS
 (Common to Power Electronics & Electric Drives/
 Power System Control & Automation/ Power & Industrial Drives/
 Power Electronics/ Electrical Power Engineering/
 Power Engineering & Energy Systems/ Power Systems(High Voltage))

Time: 3hours

Max. Marks:60

Answer any FIVE questions
All questions carry equal marks

- - -

- 1.a) Explain the need for transmission interconnections in power systems.
- b) For the system shown in figure.1b derive the equations for P & Q at both ends.

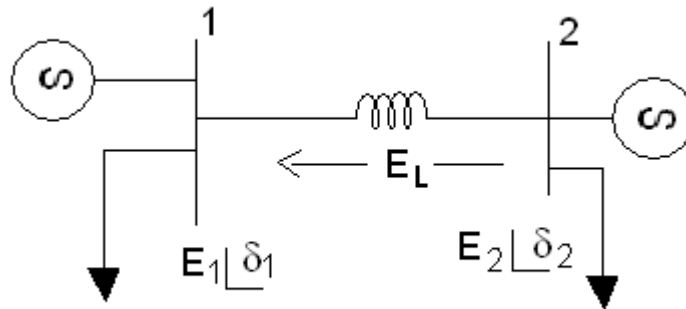


Figure 1b

- 2.a) Explain the basic concept of voltage sourced converter with the help of neat diagram.
- b) Draw the transformer connections for 48 pulse operation and explain.
- 3.a) Explain the operation of PWM voltage sourced converter.
- b) Compare voltage sourced converter with current sourced converter.
4. Briefly explain about the following objectives of shunt compensation.
 - (a) Mid point voltage regulations for line segmentation.
 - (b) Power oscillation damping.
5. Explain the following types of var generators.
 - (a) TSC
 - (b) Switching converter type var generator.

Contd....2.,

Code No: 52204/MT

::2::

- 6.a) Explain the transfer function and dynamic performance of SVC and STATCOM.
- b) Explain the operating point control scheme in SVC and STATCOM.
7. Explain the following objectives of series compensation.
 - (a) Voltage stability.
 - (b) Transient stability improvement
 - (c) Sub synchronous oscillation damping.
8. Explain the GCSC and TCSC type series compensators in detail.

* * * * *