

Code No: D109115503

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech I Semester Regular Examinations March 2010

VLSI TECHNOLOGY AND DESIGN

(Common to Embedded Systems, Digital Systems & Computer Electronics, Digital Electronics & Communication Systems, VLSI System Design / VLSI / VLSI Design, Embedded Systems & VLSI Design, VLSI& Embedded Systems, Electronics & Communication Engineering, Systems & Signal Processing)

Time: 3hours


Max.Marks:60

Answer any five questions
All questions carry equal marks

- - -

1. a) Explain the fabrication procedure for P-Well CMOS technology.
- b) What are the differences between CMOS and BiCMOS technologies in fabrication?

 2. a) Explain how to estimate propagation delay?
- b) Calculate the resistance of the polysilicon wire shown in figure. This polysilicon wire is to be fabricated with a $1\mu\text{m}$ technology. ($R_s = 4\Omega/\text{sq}$).




- c) Determine Z_{pu} / Z_{pd} for NMOS inverter driven by another inverter.

3. a) Design a symbolic layout for a complementary CMOS circuit that implements $F = \overline{A + BC}$.
- b) What are the various properties of transmission gate logic?

4. a) What are various limitations of scaling?
- b) What is via? Why these are required in circuit design.

 5. Consider the circuit shown in figure.
- Determine the logic function F.
 - Design a circuit to implement the same logic function using NOR gates.
 - Draw a transistor level schematic and use CMOS technology.



- What is clock skew? How it is calculated?
 - Explain how to optimize power for sequential circuits?
7. Explain Floor-Planning methods for a chip in detail.
8. Write short notes on
- Resistive and inductive interconnect delay.
 - High level Synthesis.
