

R09

Code No: D5607, D4904, D4303, D5404

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech II - Semester Examinations, March/April 2011

FLEXIBLE AC TRANSMISSION SYSTEMS

**(COMMON TO POWER SYSTEMS HIGH VOLTAGE, ELECTRICAL POWER
ENGINEERING, POWER ELECTRONICS, POWER ELECTRONICS & ELECTRIC
DRIVES)**

Time: 3hours

Max. Marks: 60

**Answer any five questions
All questions carry equal marks**

- - -

1. What are the constraint that limits the power flow and discuss the ways to overcome these limits. What are the benefits from the FACTS controllers? [12]
2. a) Explain the transformer connections for a 12-pulse operation of a voltage source converter.
b) What are the advantages and disadvantages of current sourced converters over voltage sourced converters. [6+6]
3. Explain the operation of 3-level voltage sourced converter in detail. [12]
4. Explain the necessity of short compensation from the view point of
 - i. Midpoint voltage regulation
 - ii. Prevention of voltage in stability
 - iii. Improvement of transient stability. [12]
5. Explain the different methods of controllable VAR generation. And also discuss about hybrid VAR generators. [12]
6. Discuss the concept of series capacitive compensation in transmission line. What is its impact on a power system? [12]
7. Discuss the principle of operation and the characteristics of a thyristor controlled reactor. [12]
8. Write notes on the following.
 - i) STATCOM
 - ii) TCSC. [12]
