

Code No: A4902

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.TECH I SEMESTER EXAMINATIONS, APRIL/MAY 2012

HVDC TRANSMISSION

(ELECTRICAL POWER ENGINEERING)

Time: 3hours

Max.Marks:60

Answer any five questions
All questions carry equal marks

- - -

1. State the advantages of HVDC transmission over EHVAC transmission for bulk power transmission.
- 2.a) Sketch the waveforms of the output voltage and the transformer secondary current in the case of 3-phase, 6-pulse bridge circuit (Graetz's circuit).
 - b) An HVDC converter rated 100 MW at 100 kV on the DC side has a commutation reactance of 0.2 p.u. The delay is varied between 5° and 20° . Determine the converter transformer rating and percentage of tap-changing required. Determine the rating of the condenser to make the p.f. on the primary side of the converter 1.0.
- 3.a) Explain the necessity of compounding both rectifier and inverter stations with constant current control.
 - b) The constants of a 3-phase line are $A=0.9 \angle 2^\circ$ and $B=0.9 \angle 70^\circ \Omega/\text{ph}$. The line delivers 60 MVA at 132 kV and 0.8 p.f. lag. Find the sending end voltage and the maximum receiving end power of the V_R are held constant. If the above line is converted into a DC line, find the receiving end power of the line.
- 4.a) Explain the operation of pulse frequency control and state why it is preferred in modern HVDC systems?
 - b) An HVDC link delivers DC power with AC line voltage to the rectifier being 400 kV and that at the inverter being 392 kV. Taking $\alpha = 10^\circ$, $\gamma = 15^\circ$ and the DC resistance of the line as 20Ω ; calculate
 - (i) The DC voltage at both the ends,
 - (ii) The current in the DC link,
 - (iii) The power delivered, and losses in the link.
- 5.a) What is the effect of different control modes on harmonics and their relative magnitudes?
 - b) Obtain relative magnitude of sixth harmonic voltage of a 6-pulse converter when $\alpha = 10^\circ$ and $\mu = 10^\circ$.
- 6.a) Why are filters not needed on the DC side with HVDC voltage source converter schemes?
 - b) Determine the cost of a 5th harmonic filter for a bipolar 4-bridge 12-pulse converter rated 1000A, ± 300 kV. The filter is connected to 400 kV, 3-ph. 50 Hz supply. Filter is to be designed for operation with one bridge out of service.
Cost: Capacitors 20 lakhs/MVAR
Inductors 45 lakhs/MVAR
Take $\alpha=15^\circ$, p.f = 0.866 and network impedance angle limited to 75° .

- 7.a) Give the principle of different types of DC circuit breaker schemes. Why is a surge diverter needed across the DC Circuit Breaker?
- b) What are the different sub harmonic oscillations that occur due to disturbances in DC systems? Explain.
8. Define and explain the following terms
- a) Two terminal HVDC system
 - b) HVDC pole
 - c) Multiterminal system
 - d) Converter substation
