

(Common To DIGITAL SYSTEMS & COMPUTER ELECTRONICS, ELECTRONICS & COMMUNICATION ENGINEERING, EMBEDDED SYSTEMS, EMBEDDED SYSTEMS & VLSI DESIGN, SYSTEMS & SIGNAL PROCESSING, VLSI & EMBEDDED SYSTEMS, VLSI SYSTEM DESIGN, DIGITAL ELECTRONICS & COMMUNICATION SYSTEMS)

Time: 3hours

Max. Marks: 60

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Implement a bcd- to excess three code converter by ROM. Calculate the cross point density of the implementation.
- b) For a pla with the following function
 $z_1(x_1x_2x_3) = x_1$: $z_2(x_1x_2x_3) = x_1x_2' + x_1'x_2$: $z_3(x_1x_2x_3) = x_2'x_3 + x_2x_3'$
 show the schematic diagram, show its ssr notation and draw nmos nor-nor implementation.
- 2.a) Explain the Boolean difference method with an example.
- b) A two level AND-OR circuit has four AND gates feeding one OR gate. The four AND gates realize the product terms $x_1x_3'x_4$, x_2x_4 , $x_1'x_3'x_4'$ and $x_1x_2x_3$ respectively. Derive the a and b - tests for detecting multiple stuck at faults.
- 3.a) Explain podem with an example.
- b) Explain transition count testing with an example.
4. Find the minimized PLA of the following output Boolean function by a PLA minimizer.
 $f_1 = (2,4,5,6,7,10,14,15)$: $f_2 = (4,5,7,11,15)$
- 5.a) Draw the portion of an ASM chart that specify a conditional operation to increment register (r) during state t1 and transfer to state t2 if control inputs z and y are equal to 1 and 0 respectively.
- b) Design an ASM chart for a serial adder with accumulator and show the control block diagram.
6. Explain the procedure of designing a fault detection experiment with the help of an example.
7. Construct a fault-detection experiment for the machine of the following table. That is entirely preset, that is with no initial adaptation part.

Ps	Ns, z	
	X = 0,	x = 1
A	D,0	c,0
B	C,0	d,0
C	A,0	b,0
D	D,1	a,1

8. Write short notes on the following.
 - a) Capabilities and limitations of FSM
 - b) Transition check approach in sequential circuits.
 - c) Bridging fault model.