

Code No: B7704

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
M.TECH II SEMESTER EXAMINATIONS, APRIL/MAY 2012
CPLD & FPGA ARCHITECTURE AND APPLICATIONS
(EMBEDDED SYSTEMS & VLSI DESIGN)

Time: 3hours

Max.Marks:60

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Compare PLA,PAL and PLD s with respect to different features, programming and applications.
- b) Give the functional description of the Altera's MAX 7000 PLD with the help of logical array block and Macro cell Diagrams.
- 2.a) Explain how Actel's ACT2 FPGA Family is architecturally close to MPGA with neat diagram.
- b) Explain how an FPGA can be chosen with different stages of Elimination trials and comparative evaluation.
- 3.a) Explain about the state assignment for FPGA
- b) Give the basic properties of petrinet Explain the traffic light controller design using petrinet notation.
- 4.a) Design a one to three pulse generation by using a PLA to generate the next state and output.
- b) Explain the application of the one Hot method to a serial 2's complement.
- 5.a) Explain one of the Mentor Graphic's FPGA advantage tool feature of state machine Design Entry.
- b) Explain the FPGA design flow with each level in the design.
- 6.a) Explain the extended petrinets for parallel controllers
- b) Explain the datapath and functional partition of FSM system level design
- 7.a) Write the HDL code for the design of 4-bit parallel adder using four 1-bit parallel adders
- b) Develop one hot state diagram for a sequence checker whose output is '1' whenever the sequence 0101 is detected. Also specify the Transition Table.
8. Write short notes on any **Two**
 - a) State machine designs centered around shift registers
 - b) Realization of State machine chart using PAL
 - c) Technology mapping for FPGAs
