R09 **Code No: D0608** JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD **M.TECH II - SEMESTER EXAMINATIONS, APRIL/MAY-2012 CMOS ANALOG AND MIXED SIGNAL DESIGN** (DIGITAL SYSTEMS AND COMPUTER ELECTRONICS)

Time: 3hours

Max. Marks: 60

Answer any five questions All questions carry equal marks

- 1.a) Draw a standard cascode current sink circuit and explain its operation and output characteristics.
 - Calculate the temperature coefficient of the Threshold referenced circuit, b) where $\binom{W}{L} = 20$, $V_{DD} = 5V$ and $R = 100k\Omega$. Assume the other required values. Resistor R is Polysilicon and has a temperature coefficient of 1500 ppm/⁰C, $\alpha = 2.3 \text{ x } 10^{-3} \text{V}/^{0} \text{C}.$
- 2.a) Show that the sensitivity of the reference circuit shown in the figure is unity.



- b) Draw a layout of current mirror circuit.
- Draw a neat current sink inverter circuit and explain the operation. 3.a)
- If $W_1 = 2\mu m$, $L_1 = 1\mu m$, $W_2 = 1\mu m$, $L_2 = 1\mu m$, $V_{DD} = 5V$, $V_{GG_1} = 3V$ for a CMOS b) current sink inverter circuit having two transistors M1 and M2. Calculate outputswing limits.
- 4. Draw the four feed back topologies and derive the expression for feedback factor and show the effect of feedback on voltage gain in all the 4 topologies.
- 5. Design an op-amp with ideal op-amp characteristics. Explain the steps, conditions and requirements to design an op-amp.
- 6.a) Explain the principle of Miller Compensation of two stage op-amp
- How can we improve the performance of open-loop comparator? b)
- 7. Explain the function of switched capacitor voltage amplifier using the parallel resistor emulation.
- 8. Write a brief note on:
 - Mixed signal layout a)
 - ADC architecture (any one has to be discussed) b)