

NR/R09

Code No: B0702/ D0702, D4902, D6402

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech II Semester Examinations, October/November 2011

ADVANCED POWER SYSTEM PROTECTION

**(COMMON TO ELECTRICAL POWER SYSTEMS, ELECTRICAL POWER
ENGINEERING, POWER ENGINEERING & ENERGY SYSTEMS)**

Time: 3hours

Max. Marks: 60

**Answer any five questions
All questions carry equal marks**

- - -

1. Explain how an Instrument Transformers can be used for the protection purpose. [12]
2. a) Explain the operation of definite time static over current relay.
b) Explain the over current relay time-current characteristics in detail. [6+6]
3. a) Realize the Angle admittance (MHO) relay using amplitude comparator.
b) Realize the Angle impedance (OHM) relay using amplitude comparator. [6+6]
4. a) Explain the operation of Elliptical relay.
b) Explain the operation of restricted reactance relay. [6+6]
5. Explain the following Pilot relaying schemes for the protection of transmission line sections.
a) Balanced voltage (opposed voltage) scheme
b) Half-wave composite scheme. [6+6]
6. Realize the Directional Over current relay using Microprocessor based scheme. [12]
7. Explain the Phase comparison carrier current protection scheme for the protection of transmission line sections. [12]
8. Write short notes on
A) Digital relaying algorithm.
B) Microprocessor based impedance relay.
C) Wire-Pilot protection. [4+4+4]
