

NR/R09

Code No: B4301 / D4301, D4201, D5401

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech II Semester Examinations, October 2011

POWER ELECTRONIC CONTROL OF AC DRIVES

**(COMMON TO POWER ELECTRONICS, POWER AND INDUSTRIAL DRIVES,
POWER ELECTRONICS & ELECTRIC DRIVES)**

Time: 3hours

Max.Marks:60

**Answer any five questions
All questions carry equal marks**

- - -

- 1.a) Derive the per phase Equivalent circuit of a 3 phase induction motor with the help of phasor diagram. (6M)
- b) Explain the Different operating regions of torque speed curve of a 3 phase induction motor. (6M)
- 2.a) Explain voltage fed current regulated inverter drive with torque and flux control of Induction Motor. (6M)
- b) Describe about Efficiency optimization control by flux program of Induction Motor Drive. (6M)
- 3.a) Derive the AC equivalent circuit of the Static Kramer's drive. (6M)
- b) Explain the operation of the static scherbius drive. (6M)
- 4.a) Discuss the Algorithm for the direct vector control process of an induction motor. (6M)
- b) Derive the functional block diagram of a current source indirect vector controller for an Induction Motor Drive. (6M)
- 5.a) Explain the different control strategies employed for Synchronous motor drive. (6M)
- b) Explain the operation of Load commutated inverter fed synchronous motor drive. (6M)
- 6.a) Briefly explain the Flux weakening operation of synchronous motor drive. (6M)
- b) Briefly explain unity power factor control of synchronous motor drive. (6M)
- 7.a) Briefly discuss constructional details and characteristics of Variable Reluctance motor drives. (6M)
- b) Explain the process of Torque production in variable reluctance motor drive. (6M)
- 8.a) Compare the Half wave and Full wave inverter based PMLD with C-dump topology. (6M)
- b) Explain the operation of current controlled Brushless dc motor Servo drive. (6M)
