

NR/R09

**Code No: A4304,A5404/C4304, C5404,C4204,
JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
M.Tech I Semester Examinations, October/November-2011
POWER ELECTRONIC CONTROL OF DC DRIVES
(COMMON TO POWER ELECTRONICS, POWER ELECTRONICS AND ELECTRIC DRIVES
POWER AND INDUSTRIAL DRIVES,)**

Time: 3 hours

Max. Marks: 60

**Answer any five questions
All questions carry equal marks**

- - -

1. Explain in detail the operation of a single phase full converter, feeding a separately excited dc motor for both continuous and discontinuous modes of operation. [12]
2. Explain the operation of a three – phase full converter drive. Also sketch and explain the output voltage and current wave forms for $\alpha = 60^0$, 90^0 and 120^0 . [12]
3. Draw the block diagram and explain the operation of a two quadrant converter-controlled separately excited dc motor drive. [12]
4. A chopper controlled dc motor has the following parameters: 200V, 6.3A, 1000rpm, $R_a = 4 \Omega$; $L_a = 0.018H$, $K_b = 1.86$ V/rad/sec. $J = 0.1$ kg – m², $B = 0.0162$ N-m/rad/sec; $f_c = 500HZ$, $V_s = 285V$ Determine
 - a) Torque - speed Characteristics for duty cycles of 0.2 and 0.6 in the forward motoring.
 - b) The average current at 500rpm, using averaging and instantaneous steady State evaluation techniques (Assume suitable duty cycle.) [12]
5. Explain in detail the dynamic simulation of the speed controlled dc motor drive. [12]
6. Explain in detail the sinusoidal pulse – width modulation control scheme for power factor improvement. Also derive the expressions for Displacement angle, Supply power factor, displacement factor and harmonic factor. [12]
7. Discuss the impact of the choice of the current controller on the dynamic performance of the dc motor drive system. [12]
8. Write short notes on the following.
 - a) Addition of free wheeling diode in three phase converters.
 - b) Sixth harmonic torque.
 - c) Hysteresis current controller. [12]

* * * * *