

Code: R7102303

**R7**

B.Tech I Year (R07) Supplementary Examinations, December 2012

**BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

(Biotechnology)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 (a) State and explain Kirchhoff's laws.  
(b) A capacitor of  $100 \mu F$  is connected across 200 V, 50 Hz single phase supply. Calculate the reactance of the capacitor, rms value of current and the maximum value of current.
- 2 (a) Explain the principles of operation of DC motor.  
(b) Explain the principle of operation of synchronous motor.
- 3 (a) Explain the principle of operation of repulsion type moving iron instruments with neat diagram.  
(b) Explain the principle and operation of induction type energy meters with neat diagram.
- 4 Explain the operation of P.N junction diode. Also explain its V-T characteristics.
- 5 Explain the concept of feedback and negative feedback of transistors.
- 6 Explain in detail class C power amplifiers.
- 7 Explain in detail:  
(a) RC phase shift oscillator.  
(b) Multivibrators.
- 8 Explain in detail the registers and counters.

\*\*\*\*\*