

**ELECTRICAL CIRCUIT ANALYSIS**

(Electrical and Electronics Engineering)


Time: 3 hours

Max Marks: 80


Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

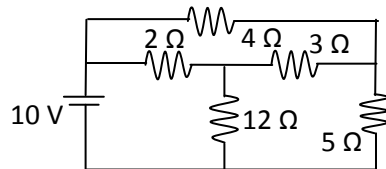- 1 (a) Explain in detail voltage and current sources.  
Find the current supplied by 10 V battery by using star delta transformation.




- 2 (a) Define co-efficient of coupling. Derive the expression for co-efficient of coupling.  
(b) A coil having an inductance of 60 MH is carrying a current of 90 A. Calculate the self induced emf in the coil, when the current is (i) reduced to zero in 0.03 sec. (ii) reversed in 0.03 sec.
- 3 (a) Derive the expression for a average value of a sinusoidal wave form.  
(b) A series RLC circuit has  $R = 5 \Omega$ ,  $L = 40 \text{ MH}$  and  $C = 1 \text{ MF}$  calculate:  
(i) Factor of the circuit. (ii) Band width.  
(iii) The resonant frequency. (iv) The half power frequencies.
- 4 (a) Derive the relation between phase and line values of a 3 - phase balanced star connected system  
(b) Three impedances each of  $(3 - j 4)$  ohm are connected in delta to a 230 V, 3-phase, 50 Hz balanced supply. Calculate the line and phone currents in delta connected load and the power delivered to the load.
- 5 Define and explain: (i) Graph. (ii) Tree. (iii) Basic cut set. (iv) Basic tieset.  
Draw th dual of the given network. And also write down the procedure to obtain the dual network.

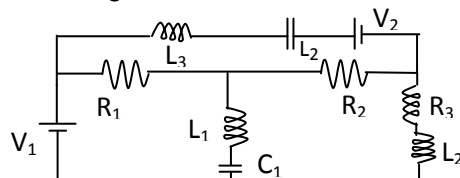


Contd. in Page 2

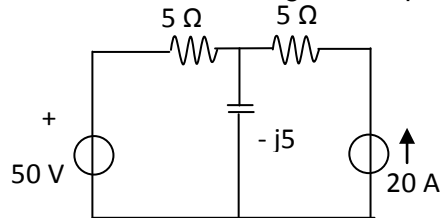- 6 (a) State and explain mill man's theorem.  
 (b) Determine the current through the capacitor using The venin's theorem.



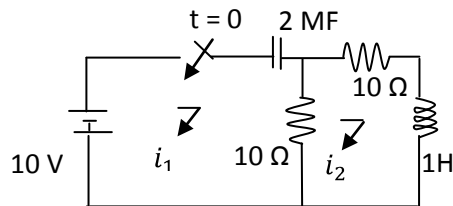- 7 For the corcuit shown the switch is closed at  $t = 0$  find the values of  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt_2}$ ,  $\frac{di_2}{dt}$ ,  $\frac{d^2i_1}{dt^2}$  and  $\frac{d^2i_2}{dt^2}$  at  $t = 0^+$ .



- 8 (a) Define and obtain hybrid parameter by taking any one example.  
 (b) A two port network has the following parameters  $Z_{11} = 20 \Omega$ ,  $Z_{12} = 5 \Omega$ ,  $Z_{21} = 20 \Omega$  and  $Z_{22} = 15 \Omega$ . calculate the short circuit parameter.

\*\*\*\*\*