R09

Code: 9A02405

B.Tech II Year II Semester (R09) Supplementary Examinations December/January 2014/2015


ANALOG ELECTRONIC CIRCUITS

(Electrical & Electronics Engineering)

Time: 3 hours Max. Marks: 70

Answer any FIVE questions All questions carry equal marks

- Design of an emitter follower for maximum efficiency. The emitter follower has $V_{CC} = -V_{EE} = 5 \text{ V}$, $R_1 = 2.15 \text{ k}\Omega$, and V_{CE} (sat) = 0.2 V. Find the optimum value of RL for maximum efficiency and find the value of this efficiency.
- 2 Derive the voltage gain, input admittance and input miller capacitance of CS amplifier using its high frequency equivalent circuit.
- 3 (a) What are series and parallel mixing and voltage, current sensing in feedback amplifiers?
 - (b) An amplifier has a voltage gain of 200, before negative feedback is applied. When negative feedback with β = 0.25 is applied, the nominal gain changes by 10%. Find the percentage change in the overall gain.
- 4 (a) Draw the RC oscillator. Using hybrid equivalent model, justify the statement that the sustained oscillations is obtained by having the gain of transistor amplifier greater than 29.
 - (b) Find the capacitor C and h_{fe} for the transistor to provide a resonating frequency of 10 kHz of a transistorized phase shift oscillator. Assume R_1 = 25 k Ω , R_2 = 60 k Ω , R_C = 40 k Ω , R = 7.1 k Ω and h_{fe} = 1.8 k Ω .
- 5 (a) Explain about power amplifiers and its features.
 - (b) Derive an expression for efficiency of class-A amplifier.
- 6 (a) The periodic ramp voltage shown below is applied to a low pass RC circuit. Find the equations from which determine the steady state output waveform.

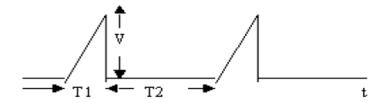

- (b) If $T_1 = T_2 = RC$, find the maximum and minimum value of the output voltage and plot this waveform.
- 7 With the help of neat wave forms explain the storage and transition times of diode.
- 8 Explain the method of unsymmetrical triggering of the binary with relevant circuit diagram.