

Code: 9A02501

R09

B.Tech III Year I Semester (R09) Regular & Supplementary Examinations December 2014

**ELECTRICAL & ELECTRONIC MEASUREMENTS**

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions

All questions carry equal marks

\*\*\*\*\*

- 1 (a) Describe the construction and working of PMMC instrument. Derive the expression for deflection.  
(b) Describe the working of a universal shunt used for multi-range ammeters. Derive the expression for resistance of different sections of a universal shunt used for a 3 range ammeter.
- 2 (a) Explain the effect of secondary burden on the ratio and phase errors of a current transformer.  
(b) Explain how power can be measured in a 3-phase circuit with the help of two wattmeters.
- 3 (a) Explain the sources of errors in a single phase induction type energy meter.  
(b) Describe the construction and working of two element induction type energy meter.
- 4 (a) Explain the term "Standardization" of a potentiometer. Describe the procedure of standardization of a d.c potentiometer.  
(b) Explain different types of AC potentiometers.
- 5 (a) Draw the circuit of a Wheatstone bridge and derive the condition for balance.  
(b) Derive the general equations for balance of a a.c bridge.
- 6 (a) Explain in detail about flux meter.  
(b) Describe the method of determining B-H curve of a magnetic material using step by step method.
- 7 (a) Describe the different parts of a CRT.  
(b) Explain the functioning of a time base generator in CRO.
- 8 (a) Explain in detail about integrating type DVM.  
(b) Describe in detail about digital frequency meter.

\*\*\*\*\*