

Code: 9A04605

B.Tech III Year II Semester (R09) Supplementary Examinations December/January 2014/2015

VLSI DESIGN

(Common to ECE, EIE and E.Con.E)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 With neat sketches explain oxidation process in IC fabrication.
- 2 (a) Write clearly about design hierarchy.
(b) Explain the concepts of regularity, modularity and locality.
- 3 Draw the CMOS NOR gate & its physical layout with stick diagram.
- 4 (a) What are the two basic forms of interconnection trees? What are the two wiring models of an interconnect? Explain them.
(b) Estimate the interconnect delay using Van Ginneken algorithm.
- 5 (a) Implement a 8-bit comparator using 4-bit comparators and other interfacing requirements.
(b) With the help of logic diagram explain the working of 4-bit comparator.
- 6 Implement the following using gate logic, switch logic and PLA in NMOS:
(i) 4:1 multiplexer. (ii) 4-bit comparator. (iii) 8-bit parity generator.
- 7 (a) Explain register transfer level synthesis.
(b) With the help of an example explain how designing is optimized at register transfer level.
- 8 (a) Explain about IDDQ (V_{DD} supply current quiescent) testing for bridging faults?
(b) Explain how a Pseudo random sequence generator and a signature analyzer is used to test an 8-input combinational circuit.
