

II B. Tech II Semester Supplementary Examinations, Dec - 2015
PULSE AND DIGITAL CIRCUITS
 (Com. to EEE, ECC)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **THREE** Questions from **Part-B**

PART -A

1. a) Why a resistive attenuator is to be compensated? Also explain how is it compensated, (3M)
- b) State clamping circuit theorem. (3M)
- c) What is a non-saturated binary and what are its advantages when compared to a saturated binary. (4M)
- d) What are the merits and demerits of ECL? (4M)
- e) Define the terms slope error and displacement error. (4M)
- f) What is a sampling gate? Mention different types of them. (4M)

PART -B

 2. a) Using relevant diagrams and wave forms explain the response of a high pass RC circuit to ramp input. Obtain the expression for its output voltage. (10M)
- b) Discuss in detail about diode storage and transition times. (6M)
3. a) Obtain the transfer characteristic for the clipper circuit shown in figure below. (10M)



- b) Explain the operation of a transistor clipper using relevant circuit diagram. (6M)
4. a) Design a monostable multivibrator with a gate width of 2 ms. (8M)
- b) Explain the operation an emitter coupled astable multi vibrator (8M)
5. a) Explain the operation of a 2 input NMOS NAND gate. (8M)
- b) Explain the operation of a CMOS NOR gate. (8M)
6. a) Explain the basic principles of Miller and Bootstrap time base generators. (10M)
- b) Define sweep time, fly back time. Derive transmission error in sweep circuits (6M)
7. a) Explain the synchronization technique with monostable multivibrator? (8M)
- b) Explain the mechanism of frequency division with astable multivibrator? (8M)

