

## III B. Tech I Semester Regular Examinations, November - 2015

## POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. Answering the question in **Part-A** is compulsory

3. Answer any **THREE** Questions from **Part-B**

\*\*\*\*\*

**PART -A**

- 1 a) Define Latching and Holding currents. [4M]
- b) Discuss briefly about advantages of freewheeling diode. [4M]
- c) Discuss about line commutated inverter. [4M]
- d) Draw the variation of output voltage with respect to firing angle of three phase semi converter. [4M]
- e) Explain time ratio control of DC-DC chopper [3M]
- f) What are the applications of Inverters? [3M]

**PART -B**

- 2 a) Explain about snubber circuit and derive the condition for  $R_s$ ? [8M]
- b) What is a MOSFET? Explain its V-I characteristics briefly. Also write its advantages over other switches. [8M]
- 3 a) Explain the operation of single phase half wave converter with RL load. Draw the output voltage waveform and derive the expression for average load voltage. [8M]
- b) A single phase full-wave ac voltage controller feeds a load of  $R=20\ \Omega$  with an input voltage of 230V, 50Hz. Firing angle for both the thyristors is  $45^\circ$ . Calculate [8M]
  - (i) rms value of output voltage.
  - (iii) Average and rms current of thyristors.
- 4 a) Derive the expression for output voltage of single-phase full converter by considering source inductance. [8M]
- b) Single phase fully controlled converter is connected to a load comprised of 2ohms resistance and 0.3H inductance. The supply voltage is 230V at 50Hz. Estimate the average load voltage, average load current and input power factor for a firing angle of  $20^\circ$ . Assume continuous and ripple free load current. [8M]
- 5 Describe the working of three phase half controlled converter with R load for  $\alpha=30^\circ$  with relevant waveforms and derive the expression for average output voltage. [16M]



- 6 a) Discuss the working of a single phase bridge type cycloconverter with RL loads and for discontinuous waveform operation with neat circuit diagram and output rms voltage and current wave form for  $f_o = (1/3) f_s$ . [8M]
- b) Explain the operation of Buck-Boost chopper with relevant waveforms and derive the expression for average output voltage. [8M]
- 7 a) With a neat circuit diagram, explain the principle of operation of a single phase half bridge inverter. [6M]
- b) A single PWM full bridge inverter feeds an RL load with  $R = 10$  ohms and  $L = 10$  mH. [10M]  
If the source voltage is 120V, find out the total harmonic distortion in the output voltage and in load current. The width of each pulse is  $120^\circ$  and output frequency is 50Hz.

\*\*\*\*\*

## III B. Tech I Semester Regular Examinations, November - 2015

## POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B**

\*\*\*\*\*

**PART -A**

- 1 a) Draw and explain the transfer characteristics of MOSFET. [4M]
- b) Define firing angle. [3M]
- c) What is commutation angle or overlap angle? [3M]
- d) Draw the output voltage waveform of three phase full converter with RL load and firing angle  $90^\circ$ . [4M]
- e) What are the applications of Cyclo converters? [4M]
- f) What are the advantages of PWM techniques? [4M]

**PART -B**

- 2 a) Discuss about switching characteristics of an SCR during turn on and off. [8M]
- b) Explain the diode bridge rectifier with R load and capacitive filter with neat circuit diagram and necessary waveforms. [8M]
- 3 a) Explain RC firing circuit with suitable waveforms. [8M]
- b) A 230V, 50Hz, one-pulse SCR controlled converter is triggered at a firing angle of  $40^\circ$  and the load current extinguishes at an angle of  $210^\circ$ . Find the average output voltage and the average load current for  $R=5\ \Omega$  and  $L=2\text{mH}$ . [8M]
- 4 a) Describe the working of single phase half controlled converter for  $\alpha=30^\circ$  with relevant waveforms and derive expression for average output voltage. [8M]
- b) A 1- $\Phi$  full converter bridge is connected to RLE load. The source voltage is 230V, 50Hz. The average load current of 10A is constant over the working range. For  $R=0.4\ \Omega$  and  $L=2\text{mH}$ , compute. i) Firing angle delay for  $E=120\text{V}$  and ii) Firing angle delay for  $E=-120\text{V}$ . Indicate which source is delivered power to load in above cases. [8M]
- 5 a) Briefly explain the operation of single-phase dual converter. [6M]
- b) A 3- $\Phi$  fully controlled bridge converter is supplying DC-load of 400V, 60A from a 3- $\Phi$ , 50Hz, 660V (line) supply. If the thyristors have a voltage drop of 1.2V when conducting, then neglecting overlap, compute. [10M]
  - a) Firing angle of thyristor.
  - b) RMS value of thyristor currents.
  - c) Mean power loss in thyristors .

- 6 a) Discuss the working of a single phase bridge type cycloconverter with RL loads and for continuous waveform operation with neat circuit diagram and output rms voltage and current wave form for  $f_o = (1/4) f_s$ . [9M]
- b) Explain the operation of Boost chopper with relevant waveforms and derive the expression for average output voltage. [7M]
- 7 Explain the operation of three-phase bridge inverter for  $180^\circ$  mode of operation with aid of relevant phase and line voltage waveforms. [16M]

\*\*\*\*\*



**III B. Tech I Semester Regular Examinations, November - 2015**  
**POWER ELECTRONICS**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**

~~~~~

**PART -A**

- 1 a) Draw and explain the output characteristics of IGBT. [4M]
- b) Draw the output voltage waveform of single phase AC voltage controller with RL load. [4M]
- c) Define extinction angle. [3M]
- d) What are the applications of dual converter. [3M]
- e) Explain current limit control of DC-DC chopper. [4M]
- f) Define amplitude modulation index. [4M]

**PART -B**

- 2 a) Explain various turn-on methods of an SCR. [8M]
- b) A thyristor operating from a peak supply voltage of 400V has the following specifications: Repetitive peak current,  $I_p = 200A$ ,  $(di/dt)_{max} = 50A/\mu s$ ,  $(dv/dt)_{max} = 200V/\mu s$ . Choosing a factor of safety 2 for  $I_p$ ,  $(di/dt)_{max}$  and  $(dv/dt)_{max}$ , design a suitable snubber circuit. The minimum value of load resistance is  $10\Omega$ ? [8M]
- 3 a) What is UJT firing circuit and explain it with suitable waveforms? [8M]
- b) A single phase half controlled bridge converter is supplied a 230V, 50Hz. Determine the average load voltage for firing angle of  $60^\circ$ . If load current of 30A is continuous and constant, what is the value of load resistance? [8M]
- 4 a) Describe the working of single-phase fully controlled bridge converter in the Rectifying mode and inversion mode. And derive the expressions for average output voltage and rms output voltage. [8M]
- b) Single phase fully controlled bridge is used for obtaining a regulated converter dc output voltage. The rms value of ac input voltage is 220V and firing angle is maintained at  $30^\circ$ , so that the load current is 4A. [8M]  
 (a) Calculate the d.c. output voltage and active and reactive power input.  
 (b) Assuming load resistance remains same and if free-wheeling diode is used at the output, calculate dc output voltage. The firing angle is maintained at  $30^\circ$ .
- 5 Explain the operation of three phase fully controlled bridge converter with RL load. Draw the voltage and current waveforms for  $\alpha = 45^\circ$ . List the firing sequence of SCRs. [16M]

- 6 a) What are cycloconverters? Discuss the working of a single phase bridge type cycloconverter with R load. Sketch a neat circuit diagram and output rms voltage and current wave form for  $f_o = (1/3) f_s$ . [9M]
- b) Explain the operation of Buck chopper with relevant waveforms and derive the expression for average output voltage. [7M]
- 7 What are different applications of inverters? Explain the operation of 3ph bridge inverter for  $120^\circ$  mode of operation with aid of relevant phase and line voltage waveforms. [16M]

\*\*\*\*\*



**III B. Tech I Semester Regular Examinations, November - 2015****POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B**

\*\*\*\*\*

**PART -A**

- 1 a) Define turn off time of an SCR. [3M]
- b) Explain the principle of line commutation. [4M]
- c) Discuss the significance of source inductance. [4M]
- d) Explain circulating and non-circulating current operation in dual converters. [4M]
- e) What is a cyclo converter? [3M]
- f) Explain briefly sine triangular PWM technique. [4M]

**PART -B**

- 2 a) Explain the static V-I characteristics of a thyristors and different modes of operation. [8M]
- b) Explain the diode bridge rectifier with R load and the output voltage waveform. [8M]
- 3 a) Explain the operation of single phase AC voltage controller with R load. Draw the necessary waveforms. [8M]
- b) A 230V, 1kW electric heater is fed through a single phase AC voltage controller from 230V, 50Hz Source. Find the load power for a firing angle delay of  $70^\circ$ . Derive the expression used. [8M]
- 4 a) Derive the expressions for the following performance factors of single-phase fully Controlled bridge converter. [8M]  
(i) Input power factor (ii) Voltage ripple factor  
(iii) Active power input (iv) Reactive power input
- b) The 1-  $\Phi$  semi converter circuit is connected to a 120V, 60 Hz supply. Determine the harmonic factor, distortion factor and input power factor if delay angle is  $\alpha = \pi/2$ . [8M]
- 5 Explain the operation of three phase fully controlled bridge converter with RLE load. Draw the voltage and current waveforms for  $\alpha = 60^\circ$ . List the firing sequence of SCRs. [16M]
- 6 a) For a single phase bridge type cyclo-converter, explain the operation of the circuit when fed to R-load with the help of neat circuit diagram and relevant output waveforms for  $\alpha = 30^\circ$  and  $\alpha = 120^\circ$  for  $f_0 = 1/4 f_s$ . [10M]
- b) Discuss the methods of controlling the output voltage of a chopper. [6M]

Code No: RT31025

**R13**

**SET - 4**

- 7 a) With a neat circuit diagram, explain the principle of operation of a single phase full bridge inverter. [6M]
- b) A single phase full bridge inverter uses a uniform PWM with two pulses per half cycle for voltage control. Plot the distortion factor, fundamental component, and lower order harmonics against modulation. [10M]

\*\*\*\*\*

**2 of 2**

