

III B. Tech I Semester Regular Examinations, November - 2015
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) Make a comparison between an ideal Op-amp and a practical Op-amp. [4M]
- b) Explain the different methods used to increase the input resistance of an op-amp. [4M]
- c) Define the Op-Amp parameters: (i) Input offset voltage, V_{io} (ii) Input bias current, I_{io} . [3M]
- d) Write about 566 voltage controlled oscillator. [4M]
- e) Differentiate between active and passive filters. [3M]
- f) List important specifications of Digital to Analog converters indicating their typical values. [4M]

PART -B

- 2 a) The common mode input of a certain differential amplifier, having differential gain of 125 is $4 \sin 200\pi t$ V. determine the common mode output if CMMR 60dB. [4M]
- b) Analyze a dual input and unbalanced output BJT differential amplifier. [8M]
- c) For an op-amp PSRR is 70dB (min), CMRR is 10^5 and $A_d = 10^5$. The output voltage changes by 20V in 4 sec. Calculate (i) common mode gain (ii) slew rate. [4M]
- 3 a) An Op-Amp has a slew rate of $2V/\mu$ sec. What is the maximum frequency of an output signal of peak value 5V at which the distortion sets in due to the slew rate limitation? [4M]
- b) Explain the parameters that should be considered for ac and dc applications of an Op-Amp. [8M]
- c) Draw a neat circuit diagram of an integrator circuit. Explain its functioning with the Input-Output wave forms. [4M]
- 4 a) What are the three differential amplifier configurations? Compare and contrast these configurations. [8M]
- b) What is an instrumentation amplifier? Draw a three Op-Amp dc instrumentation amplifier and derive the expression for its output. [8M]
- 5 a) Draw the circuit of an Astable multivibrator using Op-Amp and derive the expression for its frequency of oscillations. How will you modify this circuit to have independent control of ON and OFF time durations? [8M]
- b) What is a three terminal regulator? Draw a fixed voltage regulator circuit and explain its operation. Explain how the IC 7805 can be used as a current source. [8M]

- 6 a) With the aid of a circuit diagram, explain the principle of operation of second-order low pass active filter. [8M]
b) Draw a band – pass filter circuit with its frequency response curve. Explain its working. [8M]
- 7 a) Draw the circuit diagram of dual slope integration A to D converter and state its advantages. Explain its operation with waveforms. What parameters decide its conversion speed and accuracy? [8M]
b) Discuss the following type ADCs: [8M]
i) Ramp type ADC and ii) Servo tracking ADC.

III B. Tech I Semester Regular Examinations, November - 2015
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) Briefly explain about FET differential amplifier. [3M]
- b) Explain the term 'Slew rate' and how it affects the frequency response of an Op-Amp. [4M]
- c) Explain tracking range and capture range of a PLL. [4M]
- d) Explain how IC 7805 can be used as a current source. [4M]
- e) Draw the frequency response characteristics of a notch filter. [3M]
- f) Define the terms 'Accuracy', 'Percentage Resolution' and 'settling time' of an Analog to Digital converter. [4M]

PART -B

- 2 a) Draw the circuit of BJT differential amplifier and suggest ways to improve CMRR. [4M]
- b) Consider a BJT current mirror with a nominal current transfer ratio of unity. Let the transistors have $I_s = 10^{-15}$ A, $\beta = 100$ and $V_A = 100$ V. For $I_{REF} = 1$ mA find I_0 when $V_O = 5$ V also find the output resistance. [8M]
- c) Write about level translator circuit. [4M]
- 3 a) Define the terms: PSRR, CMRR, input bias current & input offset voltage. Explain the difference between slew rate and transient response. [3M]
- b) Write about 78XX-79XX voltage regulators and explain about their use in dual power supply. [8M]
- c) Draw and explain the working of an op amp with offset-voltage compensating network. [5M]
- 4 a) With the help of a neat circuit diagram, explain the working of a logarithmic amplifier. Derive the expression for its output voltage. [8M]
- b) Draw the circuit of an Astable multivibrator using Op-Amp and derive the expression for its frequency of oscillations. How will you modify this circuit to have independent control of ON and OFF time durations? [8M]
- 5 a) Discuss with relevant circuits and waveforms the working of Monostable multivibrator using 555 timer. [8M]
- b) Draw the block diagram of a 565 PLL IC and explain its working. [8M]



- 6 a) Explain the operation of an All-pass filter. Explain why it is known as phase shift circuit. [8M]
- b) Design a band-pass active filter of second order with a mid-band voltage gain $A_{VR}=50$. Center frequency $f_{OR}=200$ Hz and Bandwidth=20 Hz. [8M]
- 7 a) Write a short note on performance specifications of a digital to analog converter. [8M]
- b) Draw the circuit of weighted resistor DAC and derive expression for output analog voltage V_o . [8M]



III B. Tech I Semester Regular Examinations, November - 2015
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) Draw the BJT current mirror circuit and briefly explain its operation. [4M]
- b) Explain the different methods used to increase the input resistance of an op-amp. [4M]
- c) Sketch and explain the circuit operation of log and antilog amplifiers. [4M]
- d) Derive expression for o/p voltage 'V₀' of dual -slope A/D converter. [4M]
- e) Explain different configurations of an active filter. [3M]
- f) Compare different types of ADCs. [3M]

PART -B

- 2 a) Draw the block diagram of the operational amplifier and briefly write about each block. [8M]
- b) Analyze the circuit of a BJT differential amplifier with emitter resistance. [8M]
- 3 a) Write about large signal voltage gain of op-amp. [3M]
- b) Define the Op-Amp parameters: (i) Input offset voltage, V_{io} (ii) Input bias current, I_{io} with a practical setup explain how these parameters can be measured. [8M]
- c) Explain frequency compensation techniques used in Op-Amps. [5M]
- 4 a) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz. If a sinewave of 1 V peak at 1000 Hz is applied to this differentiator, draw the output waveforms. [8M]
- b) Define the terms Upper and Lower Tripping Points of a Schmitt trigger. What is the significance of the two parameters? Explain the operation of a Schmitt trigger circuit using Comparator. [8M]
- 5 a) Draw the circuit of 555 timer IC in Astable mode to get output waveform with 50% duty cycle. [6M]
- b) Define the terms: i) free-running frequency f₀, (ii) lock range, (iii) capture range, and (iv) pull-in time, pertaining to PLL. [6M]
- 6 a) Explain the term 'frequency scaling' with suitable example. [8M]
- b) Design a wide band pass filter with f_L = 200 Hz, f_H = 1KHz and a pass band gain = 4. Draw the frequency response and calculate 'Q' factor for the filter. [8M]
- 7 a) Explain the operation of a multiplying DAC and mention its applications. [8M]
- b) Describe AD 670 microprocessor compatible flash converter. [8M]

III B. Tech I Semester Regular Examinations, November - 2015
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) Write about current repeater circuits. [3M]
- b) For an op-amp having slew rate of 3 V/ μ sec, what is the maximum closed loop voltage gain that can be used when the input signal varies by 0.4V in 12 μ sec. [4M]
- c) Draw and explain the ideal voltage transfer characteristics of an op-amp. [3M]
- d) Write briefly about FSK demodulators. [4M]
- e) Explain the function of Wide band reject filter. [4M]
- f) Write about the basic Digital to Analog Conversion techniques. [4M]

PART -B

- 2 a) Explain the operation of the BJT differential amplifier with constant current source. [4M]
- b) Analyze the BJT differential amplifier with dual input and balanced output. [8M]
- c) Write about cascade differential amplifier. [4M]
- 3 a) Write about the large signal operation of an op-amp. [3M]
- b) Write about the advantages and disadvantages of 78xx and 79xx series regulators. [8M]
- c) Draw and explain the working of an op amp with offset-voltage compensating network. [5M]
- 4 a) Define the terms Upper and Lower Tripping Points of a Schmitt trigger. What is the significance of the two parameters? Explain the operation of a Schmitt trigger circuit using Comparator. [8M]
- b) Draw a neat circuit diagram of an integrator circuit. Explain its functioning with the Input-Output wave forms. Derive the output voltage V_0 of an integrator circuit. [8M]
- 5 a) What is the principle of PLL? Draw the block schematic and explain the same. [8M]
- b) Discuss about any two applications of 555 timer monostable multivibrator. [8M]
- 6 a) Design a second order low-pass Butterworth filter with a cut-off frequency of 12KHz and unity gain at low frequency. Also determine the voltage transfer function magnitude in dB at 15Hz for the filter. [8M]
- b) Given a bandpass filter with resonant frequency f_r of 1000 Hz and a bandwidth of 3000Hz; Find its (i) quality factor, (ii) lower cutoff frequency and higher cutoff frequency. [8M]
- 7 a) Sketch and explain the transfer characteristic of a DAC with necessary equations. [7M]
- b) Give the schematic circuit diagram of successive approximation type A/D converter and explain the operation of this system. [9M]

||''''||''''||